

## Teeme ise protsessori ehk kuidas progeda rauda

Anti Sullin


<http://emperor.dyn.ee>

Tevalo elektroonikahuviliste kokkutulek 2006
 
## Programmeeritav loogika

- PLD [programmable logic device]
- PLA [programmable logic array]
- PAL [programmable array logic]


AND-OR massiiv, mõnel ka trigerid väljundis. Tavaliselt püsimaluga. Realiseerib kuni mõnisada loogikaelementi. Sobib loogikafunktsioonide realiseerimiseks, sügav loogika vajab väliseid tagasisideühendusi.


 
## Programmeeritav loogika (2)

- CPLD [Complex Programmable Logic Device]


Hulk PLD sõlmesid + programmeeritavad ühendused. Tavaliselt püsimaluga (Flash). Realiseerib mõnituhat loogikaelementi. Programmeeritavad ühendused võimaldavad mõningast tagasisidet. I/O blokid võimaldavad programmeeritavaid ja/või kahesuunalisi ühendusi


 
## Programmeeritav loogika (3)

- FPGA [field programmable gate array]

Loogikamassiivide maatriks koos väga mitmekülselt programmeeritavate ühendustega. Võimaldab väga sügavat loogikat ja suurel määral tagasisidestatud süsteemide realiseerimist. Tavaliselt muutmäluga. Realiseerivad kümneid tuhandeid kuni miljoneid loogikaelemente, sisaldavad lisaks veel riistvaralisi registreid, korruteid, summaatoreid jne.



## VHDL [VHSIC Hardware Description Language]

- Programmeerimiskeel
- Süntaksi poolest Ada järglane
- Sünteesitav süntaks vs simuleeritav süntaks
- Moodulite tugi
  - Lihtne koodi partitsioneerimine ja taaskasutamine
- Riistvara paralleelsuse tugi
- Avalik standard: IEEE 1076 1987/93/02

## VHDL [VHSIC Hardware Description Language]

- Erinevad kirjeldustasemed:
  - Käitumuslik
  - Registersiirete tase
  - Boole'i võrrandid
  - Loogikalülid
- Top-Down disaini meetodikate kasutamine
  - Käitumuslikul tasemel spetsifitseerimine programmina
  - Testimine ja valideerimine käitumusliku taseme suhtes koos simuleerimisega

## Sünteesitav kood

- Ajalised viited ei ole sünteesitavad
- Muutujate tüübid on piiratud
- Keeruline aritmeetika ei ole toetatud
  - Tuleb ise teha bitthaaval
- Sünteesida ei saa jadamisi täidetavat koodi

## Muutujad riistvaras


1. Muutuja == sünkroonne triger (Flip-flop):
  - kui muutujat omistatakse mingi signaali frondil
2. Muutuja == asünkroonne triger (Latch):
  - kui muutuja väärtus ei ole programmi igas harus määratud, st igas harus ei omistata
3. Muutuja == juhe
  - kui muutuja on igas harus määratud teiste muutujate poolt (st mälu ei ole vaja)

## Varjatud registre probleem

- Kõik koodi harud peavad olema kaetud
  - ka need, kuhu kood mitte kunagi ei saa sattuda!
  - kasutades mitmevalentset loogikat, ka kõik erinevad loogikanivood!
- Lahendus: igas if / switch konstruktsioonis kasutada else haru.
- Vahetulemusi ei tohi arvutada tingimuslikus harus:
  - paralleelse loogika sünteesil ei mängi omistamiste järjekord mingit rolli!

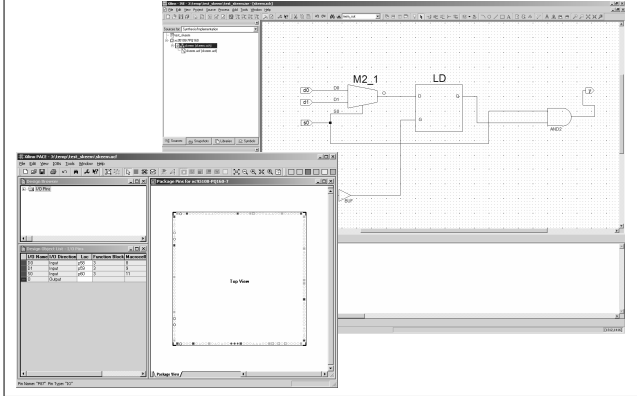
## Esimene näide

- Riistvara süntees kasutades skeemiredaktorit.



## Teine näide

- Riistvara süntees VHDL'is

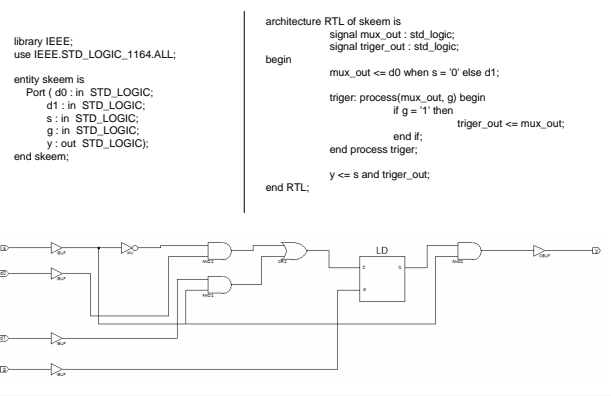

## Kolmas näide

- Keerulisem riistvara – protsessorikene
  - 4-bit andmesiin
  - 4-bit i/o aadressisiin
  - 8-bit programmimälu aadressisiin
  - 16 registrit
  - 16 sõna muutmälu
  - 1 IPC
  - MOV, AND, OR, NOT, ADD, ADC, SUB, SBC, IN, OUT, LDI, LD, ST, JMP, JZ, JNZ

## Materjale

- The VHDL Cookbook  
<http://tams-www.informatik.uni-hamburg.de/vhdl/doc/cookbook/VHDL-Cookbook.pdf>
- XESS Inc näidiskoodid  
<http://www.xess.com/>
- OpenCores: LGPL hardware  
<http://www.opencores.org/>

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity system is
    Port ( reset : in STD_LOGIC;
          addrled : out STD_LOGIC_VECTOR (6 downto 0);
          led : out STD_LOGIC_VECTOR (6 downto 0);
          clkled : out STD_LOGIC;
          clk : in STD_LOGIC);
end system;

architecture Behavioral of system is

    signal count : STD_LOGIC_VECTOR (3 downto 0);
    signal led_n : STD_LOGIC_VECTOR (6 downto 0);
    signal addrled_n : STD_LOGIC_VECTOR (6 downto 0);

    signal addr : STD_LOGIC_VECTOR (7 downto 0);
    signal cmd : STD_LOGIC_VECTOR (11 downto 0);
    signal port_id : STD_LOGIC_VECTOR (3 downto 0);
    signal inputport : STD_LOGIC_VECTOR (3 downto 0);
    signal outputport : STD_LOGIC_VECTOR (3 downto 0);
    signal pclk : STD_LOGIC;
    signal in_strobe : STD_LOGIC;
    signal out_strobe : STD_LOGIC;

    signal counter : STD_LOGIC_VECTOR (26 downto 0);

    component mem
        port(
            A : in std_logic_vector(7 downto 0);
            SPO : out std_logic_vector(11 downto 0));
    end component;

    component cpu
        Port ( addr : out STD_LOGIC_VECTOR (7 downto 0);
              cmd : in STD_LOGIC_VECTOR (11 downto 0);
              port_id : out STD_LOGIC_VECTOR (3 downto 0);
              inputport : in STD_LOGIC_VECTOR (3 downto 0);
              outputport : out STD_LOGIC_VECTOR (3 downto 0);
              clk : in STD_LOGIC;
              reset : in STD_LOGIC;
              in_strobe : out STD_LOGIC;
              out_strobe : out STD_LOGIC);
    end component;

    begin
        clkled<=pclk;
        addrled<=not addrled_n;
        led<=not led_n;

        process (out_strobe, pclk)
        begin
            if pclk'event and pclk='1' then
                if out_strobe='1' then
                    count <= outputport;
                end if;
            end if;
        end process;

        processor:cpu
        port map(
            addr => addr,
            cmd => cmd,
            port_id => port_id,
            inputport => inputport,
            outputport => outputport,
            clk => pclk,
            reset => reset,
            in_strobe => in_strobe,
            out_strobe => out_strobe);

    program:mem
        port map(
            A => addr,
            SPO => cmd);

    LEDs: process(count)
        begin
            case count is
                when "0000" => led_n <= "0111111";
                when "0001" => led_n <= "0000110";
                when "0010" => led_n <= "1011011";
                when "0011" => led_n <= "1001111";
                when "0100" => led_n <= "1100110";
                when "0101" => led_n <= "1101101";
                when "0110" => led_n <= "1111101";
                when "0111" => led_n <= "0000111";
                when "1000" => led_n <= "1111111";
                when "1001" => led_n <= "1101111";
                when "1010" => led_n <= "1110111";
            end case;
        end process;

        when "1011" => led_n <= "1111100";
        when "1100" => led_n <= "0111001";
        when "1101" => led_n <= "1011110";
        when "1110" => led_n <= "1111001";
        when others => led_n <= "1110001";
    end case;
end process LEDs;

ADDRLEDS: process(addr)
begin
    case addr(3 downto 0) is
        when "0000" => addrled_n <= "0111111";
        when "0001" => addrled_n <= "0000110";
        when "0010" => addrled_n <= "1011011";
        when "0011" => addrled_n <= "1001111";
        when "0100" => addrled_n <= "1100110";
        when "0101" => addrled_n <= "1101101";
        when "0110" => addrled_n <= "1111101";
        when "0111" => addrled_n <= "0000111";
        when "1000" => addrled_n <= "1111111";
        when "1001" => addrled_n <= "1101111";
        when "1010" => addrled_n <= "1110111";
        when "1011" => addrled_n <= "1111100";
        when "1100" => addrled_n <= "0111001";
        when "1101" => addrled_n <= "1011110";
        when "1110" => addrled_n <= "1111001";
        when others => addrled_n <= "1110001";
    end case;
end process ADDRLEDS;

clockhz: process (clk)
begin
    if clk'event and clk='1' then
        if counter<7999999 then
            counter<=counter+1;
        else
            counter<=(others=>'0');
            pclk<=not pclk;
        end if;
    end if;
end process clockhz;

end Behavioral;

```

```

signal writereg : std_logic_vector(15 downto 0);
signal reg_1 : std_logic_vector(3 downto 0); -- reg 1 address
signal reg_2 : std_logic_vector(3 downto 0); -- reg 2 address
signal reg_in_sel : std_logic_vector (1 downto 0);

signal mem : bus4(15 downto 0);
signal mem_in : std_logic_vector(3 downto 0);
signal mem_out_1 : std_logic_vector(3 downto 0);
signal mem_1 : std_logic_vector(3 downto 0); -- mem rd address
signal writemem : std_logic_vector(15 downto 0);

signal const : std_logic_vector(3 downto 0);

signal reset_delay : std_logic;
signal internal_reset : std_logic;

begin
    -- RESET LOGIC
    -- internal reset f/f-s - reset delay for startup
    process (clk, reset)
    begin
        if reset = '1' then
            reset_delay<='1';
        else
            if clk'event and clk='1' then
                reset_delay<='0';
            end if;
        end if;
    end process;

    process (clk, reset)
    begin
        if reset = '1' then
            internal_reset<='1';
        else
            if clk'event and clk='1' then
                if reset_delay='0' then
                    internal_reset<='0';
                else
                    internal_reset<='1';
                end if;
            end if;
        end if;
    end process;

    -- PROGRAM COUNTER REGISTER & FLAGS REGISTER
    process (clk, internal_reset)
    begin
        if internal_reset = '1' then
            pc <= (others => '0');
            z <= '0';
        else
            if clk'event and clk='1' then
                pc<=next_pc;
                if writec='1' then
                    c<=alu_c;
                end if;
                if writes='1' then
                    z<=alu_z;
                end if;
            end if;
        end if;
    end process;
    addr<=pc;

    -- REGISTER FILE
    -- 16 registers, 4bit each
    gl: for cnt in 0 to 15 generate
        process (clk, internal_reset)
        begin
            if internal_reset = '1' then
                reg(cnt)<=(others=>'0');
            else
                if clk'event and clk='1' then
                    if writereg(cnt)='1' then
                        reg(cnt)<=reg_in;
                    end if;
                end if;
            end process;
        end generate;

        -- register file demux
        -- if cmd output goes to register, this array has register's
        enable signals
        outdemux <= "1000000000000000" when cmd(7 downto 4) = "1111"
        else
            "0100000000000000" when cmd(7 downto 4) = "1110" else
                "0010000000000000" when cmd(7 downto 4) = "1101" else
                    "0001000000000000" when cmd(7 downto 4) = "1100" else
                        "0000010000000000" when cmd(7 downto 4) = "1011" else
                            "0000001000000000" when cmd(7 downto 4) = "1010" else
                                "0000000100000000" when cmd(7 downto 4) = "1001" else
                                    "0000000010000000" when cmd(7 downto 4) = "1000" else
                                        "0000000001000000" when cmd(7 downto 4) = "0111" else
                                            "0000000000100000" when cmd(7 downto 4) = "0110" else
                                                "0000000000010000" when cmd(7 downto 4) = "0101" else
                                                    "0000000000001000" when cmd(7 downto 4) = "0100" else
                                                        "0000000000000100" when cmd(7 downto 4) = "0011" else
                                                            "0000000000000010" when cmd(7 downto 4) = "0010" else
                                                                "0000000000000001" when cmd(7 downto 4) = "0001" else
                                                                    "0000000000000000";

        -- register file outputs (multiplexers)
        reg_out_1 <= reg(0) when reg_1 = "0000" else
            reg(1) when reg_1 = "0001" else
                reg(2) when reg_1 = "0010" else
                    reg(3) when reg_1 = "0011" else
                        reg(4) when reg_1 = "0100" else
                            reg(5) when reg_1 = "0101" else
                                reg(6) when reg_1 = "0110" else
                                    reg(7) when reg_1 = "0111" else
                                        reg(8) when reg_1 = "1000" else
                                            reg(9) when reg_1 = "1001" else
                                                reg(10) when reg_1 = "1010" else
                                                    reg(11) when reg_1 = "1011" else
                                                        reg(12) when reg_1 = "1100" else
                                                            reg(13) when reg_1 = "1101" else
                                                                reg(14) when reg_1 = "1110" else
                                                                    reg(15);

        reg_out_2 <= reg(0) when reg_2 = "0000" else
            reg(1) when reg_2 = "0001" else
                reg(2) when reg_2 = "0010" else
                    reg(3) when reg_2 = "0011" else
                        reg(4) when reg_2 = "0100" else
                            reg(5) when reg_2 = "0101" else
                                reg(6) when reg_2 = "0110" else
                                    reg(7) when reg_2 = "0111" else
                                        reg(8) when reg_2 = "1000" else
                                            reg(9) when reg_2 = "1001" else
                                                reg(10) when reg_2 = "1010" else
                                                    reg(11) when reg_2 = "1011" else
                                                        reg(12) when reg_2 = "1100" else
                                                            reg(13) when reg_2 = "1101" else
                                                                reg(14) when reg_2 = "1110" else
                                                                    reg(15);

        -- REG FILE IN MUX
        -- data can be stored to register file from 4 sources depending
        -- the command
        process (alu_r, mem_out_1, inputport, const, reg_in_sel)
        begin
            case reg_in_sel is
                when "01" => reg_in <= mem_out_1; -- reg <= mem
                when "10" => reg_in <= inputport; -- reg <= input port
                when "11" => reg_in <= const; -- reg <= constant
            end case;
            value in command
            when others => reg_in <= alu_r; -- reg <= alu result
        end process;

        -- RAM
        -- RAM registers: 16 words, 4 bits each
        process (clk, internal_reset)
        variable cnt : integer range 0 to 15;
        begin
            if internal_reset='1' then
                for cnt in 0 to 15 loop
                    mem(cnt)<=(others=>'0');
                end loop;
            else
                if clk'event and clk='1' then
                    for cnt in 0 to 15 loop
                        if writemem(cnt)='1' then
                            mem(cnt)<=mem_in;
                        end if;
                    end loop;
                end if;
            end process;
        end process;
    end process;

```

```

end if;
end process;

-- RAM output demux
mem_out_1 <= mem(0) when mem_1 = "0000" else
mem(1) when mem_1 = "0001" else

mem(2) when mem_1 = "0010" else
mem(3) when mem_1 = "0011" else
mem(4) when mem_1 = "0100" else
mem(5) when mem_1 = "0101" else
mem(6) when mem_1 = "0110" else
mem(7) when mem_1 = "0111" else
mem(8) when mem_1 = "1000" else

mem(9) when mem_1 = "1001" else

mem(10) when mem_1 = "1010" else
mem(11) when mem_1 = "1011" else
mem(12) when mem_1 = "1100" else
mem(13) when mem_1 = "1101" else
mem(14) when mem_1 = "1110" else
mem(15);

mem_in<=reg_out_1;

-----
-- ALU - ARITHMETIC AND LOGIC UNIT

-- ADDER / SUBTRACTER
-- one adder is here, its input and output is switched below for
multiple functions
process (add_x, add_y, add_c)
begin
-- result has one extra bit - carry out
add_r <= ('0'&add_x) + ('0'&add_y) + ('0000'&add_c);
end process;

-- ALU CORE
process (alu_x, alu_y, c, alu_op, add_r)
begin
alu_c <= '0'; --default carry flag

add_x <= alu_x; -- default adder connections
add_y <= alu_y; -- everything must be always connected
somewhere
add_c <= c;

-- actual alu result is multiplexed from different
-- functional blocks depending on the command given
case alu_op is
when "000" => alu_r <= alu_y; -- mov: r <=
y
when "001" => alu_r <= alu_x and alu_y; -- and: r <=
x and y
when "010" => alu_r <= alu_x or alu_y; -- or: r<= x
or y
when "011" => alu_r <= not alu_y; --
not: r<=not y
when "100" => -- add:
(r,c) <= x + y
add_c <= '0';
alu_r <= add_r(3 downto 0);
alu_c <= add_r(4);
when "101" => -- addc:
(r,c) <= x + y + c
alu_r <= add_r(3 downto 0);
alu_c <= add_r(4);
when "110" => -- sub:
(r,c) <= x - y
add_c <= '1';
add_y <= not alu_y;
alu_r <= add_r(3 downto 0);
alu_c <= add_r(4);
when others => -- subc:
(r,c) <= x - y - c
add_c <= not c;
add_y <= not alu_y;
alu_r <= add_r(3 downto 0);
alu_c <= add_r(4);
end case;
alu_r <= alu_r(3) or alu_r(2) or alu_r(1) or alu_r(0); -- next
zero flag
end process;

-- ALU input is hardwired to register file output at the moment
alu_x <= reg_out_1;
alu_y <= reg_out_2;

-----
-- PROCESSOR CORE - COMMAND DECODER UNIT
process (cmd, pc, z, outdemux)
begin
-- default values (can be changed later, nothing can be left
unconnected)
writereg <= (others => '0'); -- no bits are latched to
register
register
writemem <= (others => '0'); -- no bits are latched to memory
next_pc <= pc + 1; -- next
command address
in_strobe <= '0';
out_strobe <= '0';
reg_in_sel <= "00"; -- register file input
port is connected to alu output
writec <= '0'; -- disable latching
flags on next clock
writez <= '0';

if cmd(11)='0' then
writereg <= outdemux; -- alu op - every command writes to
register file register selected by outdemux (=x)
writec <= '1'; -- every
command updates flags
writez <= '1';
else
case cmd(10 downto 8) is -- not alu command
when "000" => -- read data from in port
in_strobe <= '1'; -- indicate external hardware that read
occurs on next clk
reg_in_sel <= "10"; -- switch register file input to
external input
writereg <= outdemux;
when "001" => -- write data to out port
out_strobe <= '1'; -- indicate external hardware to
read data from output port on next clk
when "010" => -- load immediate
reg_in_sel <= "11"; -- switch reg file input to
immediate operand from command code
writereg <= outdemux;
when "011" => -- load mem
reg_in_sel <= "01"; -- switch reg file input to
memory output
writereg <= outdemux;
when "100" => -- store mem
writemem <= outdemux; -- enable latching data at given
memory address
when "101" => -- jmp
next_pc <= cmd(7 downto 0);
when "110" => -- jmp zero
if z='1' then -- conditional jump
next_pc <= cmd(7 downto 0);
end if;
when others => -- (111) jmp not zero
if z='0' then -- conditional jump
next_pc <= cmd(7 downto 0);
end if;
end case;
end if;
end process;

-- other direct connections
const <= cmd(3 downto 0);
outputport<=reg_out_1;
port_id <= cmd(7 downto 4);
reg_1 <= cmd(7 downto 4);
reg_2 <= cmd(3 downto 0);
mem_1 <= cmd(3 downto 0);
alu_op <= cmd(10 downto 8);
end Behavioral;

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mem IS
port (
a: IN std_logic_VECTOR(7 downto 0);
spo: OUT std_logic_VECTOR(11 downto 0));
END mem;

ARCHITECTURE mem_a OF mem IS
begin
cntr: process(a)
begin
case a is
when "00000000" => spo <= "101000010001";
when "00000001" => spo <= "101000000000";
when "00000010" => spo <= "010000000001";
when "00000011" => spo <= "100100000000";
when others => spo <= "110100000010";
end case;
end process cntr;
END mem_a;

```